



12.1 Current Electricity & 12.2 Electric Currents

Learning Goals:

- ❑ I can define the following terms and state how they apply to common devices, such as a flashlight: current electricity, source, electric circuit, load, switch
- ❑ You will be able to apply the above terms to common devices such as the flashlight
- ❑ I can state examples of good conductors

Electron Flow

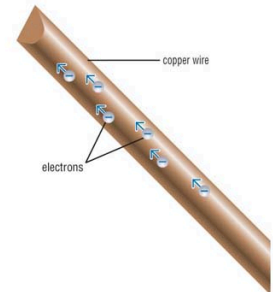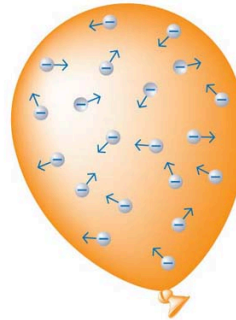- ❖ **Static Electricity:** an imbalance of electric charge on an object, sometimes resulting in an electric discharge



- ❖ **Current Electricity** is the _____
through a _____.

When we have an electric discharge during static electricity (shocks, lightning), it is:

- ❖ An _____ and _____ path
- ❖ Occurs for a very _____ period of time

The flow of electrons in current electricity is:

- ❖ _____
- ❖ moving for much _____
- ❖ directed to power devices

Electrons

_____ through a conductor. Examples of good conductors include:

*Human skin is a fair conductor


Good Conductors	
Silver	Copper
Gold	Aluminum
Magnesium	Tungsten
Nickel	Mercury
Platinum	Iron

- ❖ In order to make electrons flow, we need _____ of electrical energy, such as a _____ or a _____.
- ❖ If you are missing this source, then electrons will _____ and the object will not work
- ❖ Ex: dead batteries, power outages



Electric Circuit

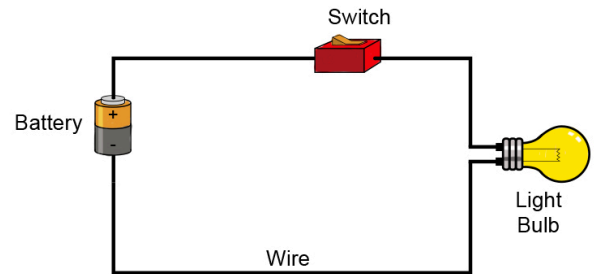
- ❖ Electronic devices require a _____ in order to function
- ❖ An **electric circuit** is a _____ for electrons to flow.
- ❖ A simple electric circuit includes:
 1. _____ (battery)
 2. _____ (light bulb)
 3. _____
 4. _____ (optional on/off switch)



1. **Source:** can be as _____ and _____ as a battery, or as _____ as a generating station
2. **Load:** a device that _____ electrical energy into other usable forms of energy.
 - ❖ Examples of this include: _____.
3. **Conducting wires:** _____ all the parts of an electric circuit together.
 - ❖ Provide a pathway for electrons to flow between component
 - ❖ Typically made of _____

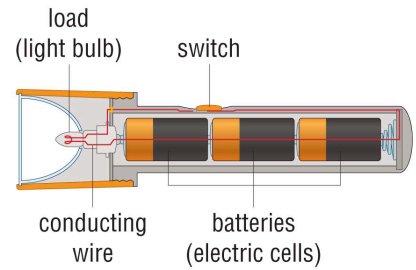4. **Switch:** controls the flow of electrons in an electric circuit by _____ the circuit.

- ❖ When a switch is *on* then the circuit is _____
- ❖ When a switch is *off*, the circuit is _____ and the path for electron flow is _____
- ❖ When the pathway is broken or incomplete, there is no _____



SUMMARY

- ❖ Static electricity involves the movement of electrons in an _____ way
- ❖ Current electricity involves the _____ flow of electrons through a _____
- ❖ Current electricity requires a _____ of electrical energy to create a _____
- ❖ An electric circuit is a _____ that allows electrons to flow
- ❖ An electric circuit is made up of an energy source, conducting wires, a load and a switch

Homework

- ☐ Watch consolidation video > Physics > Module 8
- ☐ Read 12.1 p.507-508, Complete # 1-6
- ☐ Read 12.2 p.509-510, Complete #1-6